

**Total No of Questions: [12]**

**SEAT NO. :**

**[Total No. of Pages : 3 ]**

**FE 2008 COURSE  
BASIC ELECTRICAL ENGINEERING**

**Time: 3 Hours**

**Max. Marks : 100**

*Instructions to the candidates:*

- 1) *Answers to the two sections should be written in separate answer books.*
- 2) *Neat diagrams must be drawn wherever necessary.*
- 3) *Figures to the right side indicate full marks.*
- 4) *Use of Calculator is allowed.*
- 5) *Assume Suitable data if necessary*

**SECTION I**

- Q.1 (a) Define Resistance Temperature Coefficient (RTC). State its unit. With usual notations prove that **8M**

$$\alpha_2 = \alpha_1 / [1 + \alpha_1 (t_2 - t_1)]$$

- (b) An electric pump lifts 12 m<sup>3</sup> of water per minute to a height of 15 meters. If its overall efficiency is 60 %, find the input power. If the pump is used for 4 hours a day find the cost of energy for the month of April. **8M**

**OR**

- Q.2 (a) Define insulation resistance & Derive its expression for single core cable. **8M**

- (b) With neat sketch explain construction & working of Lead Acid Battery. **8M**

- Q.3 (a) State & Prove maximum power transfer theorem as applied to a d c resistive circuit. **8M**

- (b) Obtain the equations to convert delta connected resistive network into equivalent star connected network. **8M**

**OR**

- Q.4 (a) State & explain Kirchoff's laws as applied to a d c circuit. **8M**

- (b) State & explain Superposition Theorem as applied to a d c circuit. **8M**

- Q.5 (a) Compare Electric circuit with magnetic circuit stating clearly the similarities & dissimilarities. **8M**

- (b) Define self inductance of a coil. & hence state the factors that affect its value. **4M**

- (c) The length of an air cored solenoid is 1.7 m & area of cross section is 12 cm<sup>2</sup>. The number of turns of the coil is 1000. Calculate- **6M**

- a) the self inductance    b) the energy stored in the magnetic field when a current of 10 A flows through the coil.

**OR**

- Q.6 (a) Define & state units of i) Reluctance ii) MMF **8M**  
 iii) Magnetic flux density iv) permeance
- (b) Compare statically induced emf & Dynamically induced emf **4M**
- (c) Define coefficient of coupling & Derive expression for it. **6M**

## SECTION II

- Q.7 (a) Define Average value of sinusoidally varying quantity. Derive its expression in terms of its peak value. **8M**
- (b) Two capacitors of  $8\ \mu\text{f}$  &  $2\ \mu\text{f}$  are connected in series across 400 V supply. Calculate i) resultant capacitance ii) charge on each capacitor iii) voltage across each capacitor. **6M**
- (c) Define & state the units of - i) Electric flux density ii) Electric field intensity **4M**

## OR

- Q.8 (a) Define RMS value of sinusoidally varying quantity. Derive its expression in terms of its peak value. **8M**
- (b) An alternating current is given by  $i = 14.14 \sin 377t$ . Find i) RMS value of current **6M**  
 ii) Frequency iii) instantaneous value of current at  $t = 3$  msec. Assume wave starts from origin & increasing positively.
- (c) Define – i) Form factor ii) Peak factor **4M**
- Q.9 (a) A series R-L-C circuit has resistance of 50 ohms, inductance of 0.1 H & capacitance of  $50\ \mu\text{f}$  connected in series across single phase 230 V, 50 Hz supply. Calculate – i) current drawn by circuit ii) power factor of circuit iii) active and reactive power consumed by the circuit. **8M**
- (b) Define the terms – i) admittance ii) conductance iii) susceptance as related to a c circuit. State their units. Draw admittance triangle. **8M**

## OR

- Q.10 (a) Two impedances  $(8+j6)\ \Omega$  &  $(3-j4)\ \Omega$  are connected in parallel. If the total current drawn by combination is 25 A at unity power factor, find the current and power taken by each impedance. **8M**
- (b) Sketch the waveform of voltage, current & power if  $v = V_m \sin \omega t$  volts is applied across R-L series circuit. Derive the expression of current in this case. Also **state** the expression of power in this case. **8M**
- Q.11 (a) Write short notes on - i) Losses in transformer ii) Dimmerstat **8M**
- (b) Three identical coils each having resistance of  $10\ \Omega$  & inductance of 0.03 H are connected in delta across a three phase 400 V, 50 Hz supply. Calculate –  
 i) Phase current ii) line current iii) total power consumed by load. **8M**

**OR**

- Q.12 (a) With the help of neat circuit diagram describe the method of performing direct load test on a single phase transformer. Explain how efficiency & regulation can be calculated in this case. **8M**
- (b) Derive the emf equation of single phase transformer. **4M**
- (c) **State** the relationship between line value & phase value of voltage and current for 3 phase **star connected load**. Also **state** the expression for active power and reactive power. **4M**

\*\*\*\*\*