

Total No. of Questions : 12]

[Total No. of Printed Pages : 4

[3861]-154

F. E. (Semester - I) Examination - 2010

BASIC ELECTRICAL ENGINEERING

(2008 Pattern)

Time : 3 Hours]

[Max. Marks : 100

Instructions :

- (1) Answers to the **two sections** should be written in **separate answer-books**.
- (2) Answer Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4, Q. No. 5 or Q. No. 6, Q. No. 7 or Q. No. 8, Q. No. 9 or Q. No. 10 and Q. No. 11 or Q. No. 12.
- (3) Figures to the right indicate full marks.
- (4) Neat diagrams must be drawn wherever necessary.
- (5) Use of non-programmable pocket size scientific calculator is permitted.
- (6) Assume suitable additional data, if necessary.

SECTION - I

- Q.1) (A) What is Insulation Resistance ? State its unit and obtain an expression for Insulation Resistance of the Cable. [08]
- (B) With neat sketch explain Construction and Working of Lead Acid Cell. [08]

OR

- Q.2) (A) A resistance element having cross-sectional area of 10 mm^2 and length of 10 meter takes a current of 4 Amp from 200V supply at temperature of 25°C . Find (i) resistivity of the material and (ii) current it will take when temperature rises to 75°C . Assume $\alpha_{25} = .0003/^\circ\text{C}$. [06]



- (B) If α_1 and α_2 are the two resistance temperature coefficients at t_1 °C and t_2 °C, then prove that $(\alpha_1 - \alpha_2) = \alpha_1 \alpha_2 (t_2 - t_1)$. [06]
- (C) State applications of Nickel-Iron Cell and Nickel-Cadmium Cell. [04]

- Q.3** (A) State and explain Superposition Theorem as applied to Simple DC Circuit. [06]
- (B) State and explain Kirchoff's Laws. [04]
- (C) Determine resistance between (x) and (y) for the circuit shown in fig. 1 : [06]

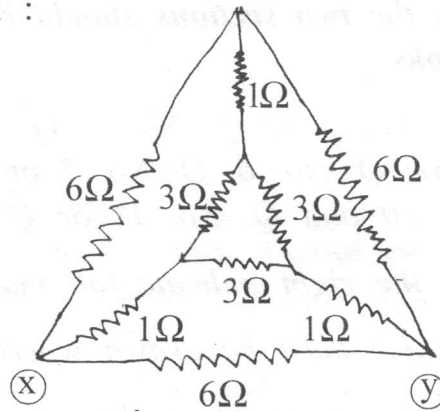


Fig. 1

OR

- Q.4** (A) State and explain Maximum Power Transfer Theorem. [06]
- (B) Apply Thevenin's Theorem to the circuit show in fig. 2 to calculate current in 01Ω resistance : [10]

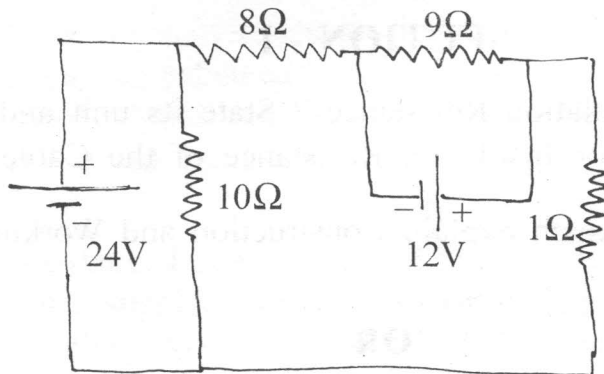


Fig. 2

- Q.5** (A) Compare Electric and Magnetic Circuit. [08]
- (B) Write short notes : [10]
- (a) Magnetic Leakage and Fringing.
- (b) Energy stored in a Magnetic Field.

OR

- Q.6) (A) Explain what do you mean by Statically Induced emf and Dynamically Induced emf ? [06]
- (B) A steel ring of 25 cm mean diameter and of circular cross-section 3 cm diameter has an air gap of 1.5 mm length. It is wound uniformly with 700 turns of wire carrying a current of 2 Amp. Calculate :
- (a) MMF
 - (b) Flux Density
 - (c) Reluctance and
 - (d) Relative Permeability of Steel Ring [12]

SECTION - II

- Q.7) (A) Define w.r.t. alternating quantities : [09]
- (a) Instantaneous Value
 - (b) Waveform
 - (c) Cycle
 - (d) Amplitude
 - (e) Periodic Time
 - (f) Frequency
- (B) Sketch Waveforms of Currents and find its rms value and average value for the equation : [08]
- (a) $i_1 = 15 \sin (314.159 t)$ and
 - (b) $i_2 = 10 \sin (314.159 t - \pi/2)$

OR

- Q.8) (A) Prove that rms value of the sinusoidal alternating current is 0.707 times its maximum value. [06]
- (B) Derive expression for energy stored in a capacitor. [06]
- (C) Two capacitors of $50\mu\text{F}$ each are connected in parallel with each other and this combination is connected in series with two capacitors of $80\mu\text{F}$ of $40\mu\text{F}$ each. Calculate equivalent capacitance of the circuit. [05]

