



F.E. (Semester – I) Examination, 2011
BASIC ELECTRICAL ENGINEERING
(2008 Pattern)

Time : 3 Hours

Max. Marks : 100

- Instructions:**
- 1) In Section – I, attempt Q. 1 or Q. 2, Q. 3 or Q. 4, Q. 5 or Q. 6. In Section – II, attempt Q. 7 or Q. 8, Q. 9 or Q. 10, Q. 11 or Q. 12.
 - 2) Answers to the **two** Sections should be written in **separate** answer books.
 - 3) Figures to the **right** indicate **full** marks.
 - 4) Neat diagrams must be drawn **wherever** necessary.
 - 5) Use of non-programmable electronic calculator is **allowed**.
 - 6) Assume suitable data, if **necessary**.

SECTION – I

1. a) With usual notations prove that 6
$$(\alpha_1 - \alpha_2) = \alpha_1 \alpha_2 (t_2 - t_1)$$

b) Two coils connected in series have resistances of $600\ \Omega$ and $300\ \Omega$ and temp. coefficient of resistance of 0.1% and 0.4% respectively at 20°C . Find the resistance of combination at a temperature of 50°C . What is the effective temperature coefficient of combination? 6
c) What are the indications which confirm that a lead acid cell is fully charged? 6

OR

2. a) Define insulation resistance and obtain an expression for insulation resistance of a single core cable. 6
b) A diesel-electric generating set supplies an output of 50 kW. The calorific value of fuel used is 12,500 k cal/kg. If the overall efficiency of the unit is 35%. (i) Calculate the mass of oil required per hour and (ii) The electrical energy generated per tonne of the fuel. 6
c) Compare lead acid cell and Nickel cadmium cell. 6
3. a) Explain the following terms with reference to dc resistive networks : 8
 - 1) Unilateral and bilateral networks
 - 2) Linear and non linear networks
 - 3) Lumped and distributed networks
 - 4) Active and passive networks.



P.T.O.



- b) Formulate the Kirchhoff's voltage law equations for the ckt of Fig. 1 and find the values of I_1 , I_2 and I_3 .

8

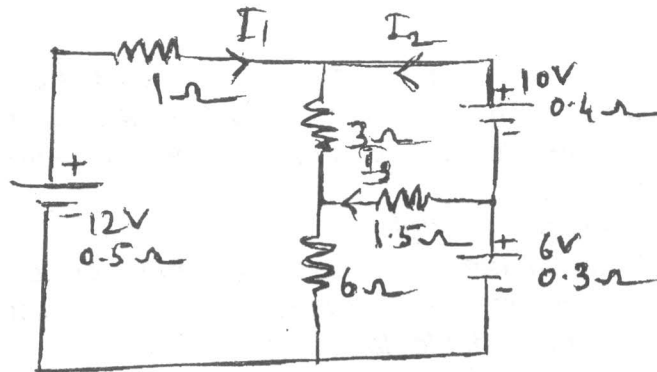


Fig. 1

OR

4. a) Derive an expression to convert Delta connected network into its equivalent star network. 8
 b) Find the current in 20Ω resistor connected across AB using Thevenin's Theorem. 8

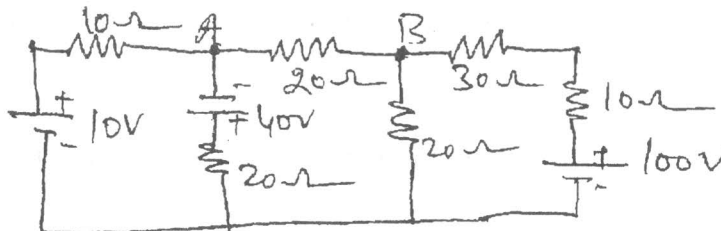


Fig. 2

5. a) Compare electric and magnetic circuits clearly stating similarities and dissimilarities between them. 8
 b) A coil of 2000 turns is wound uniformly over a nonmagnetic ring of mean circumference of 80 cm and cross sectional area of 0.6 cm^2 . If the current through the coil is 2 amperes, calculate (i) Magnetising force (ii) Reluctance (iii) Total flux (iv) Flux density. 8

OR



