



Seat No.	
-------------	--

**F.E. (Semester – I) Examination, 2014**  
**BASIC ELECTRICAL ENGINEERING**  
**(Old) (2008 Course)**

Time : 3 Hours

Max. Marks : 100

- Instructions :** 1) Attempt Q. No. 1 or 2, Q. No. 3 or 4, Q. No. 5 or 6, Q. No. 7 or 8, Q. No. 9 or 10, Q. No. 11 or 12.  
2) Answer to the **two** Sections must be written **separate** answer-books.  
3) Figures to the **right** indicate **full** marks.  
4) **Use** of non-programmable pocket size scientific calculator is **permitted**.  
5) **Neat** diagrams must be drawn **wherever** necessary.  
6) Assume suitable data, **if necessary**.

SECTION – I

1. a) A specimen of copper wire has its resistance equal to 4 mΩ and its temp. coefficient of resistance equal to  $\left[\frac{1}{234.5}\right]$  per °C. Find its resistance and temp. coefficient of resistance at 70°C and 100°C. **8**
- b) Define insulation resistance and obtain an expression for it of a single core cable. **8**
- OR
2. a) If  $\alpha_1$  and  $\alpha_2$  are resist. temp. coefficients at  $t_1$ °C and  $t_2$ °C respectively then prove that
- i)  $\frac{\alpha_1}{\alpha_2} = 1 + \alpha_1(t_2 - t_1)$  and **8**
- ii)  $[\alpha_1 - \alpha_2] = \alpha_1 \alpha_2(t_2 - t_1)$  **8**
- b) An electric furnace is used in order to melt 50 Kg of tin per hour. melting temp. of tin is 235°C and room temp. is 15°C. Latent heat of fusion for tin is 13.31 KCal/Kg and specific heat of tin is 0.055 KCal/Kg °K. If input to furnace is 6 KW, find efficiency of furnace. **8**
3. a) State and explain :
- i) Kirchhoff's laws and **8**
- ii) Thevenin's theorem. **8**



- b) Calculate current flowing in  $2\Omega$  resistance for the circuit shown in Fig. 1 using superposition theorem.

8

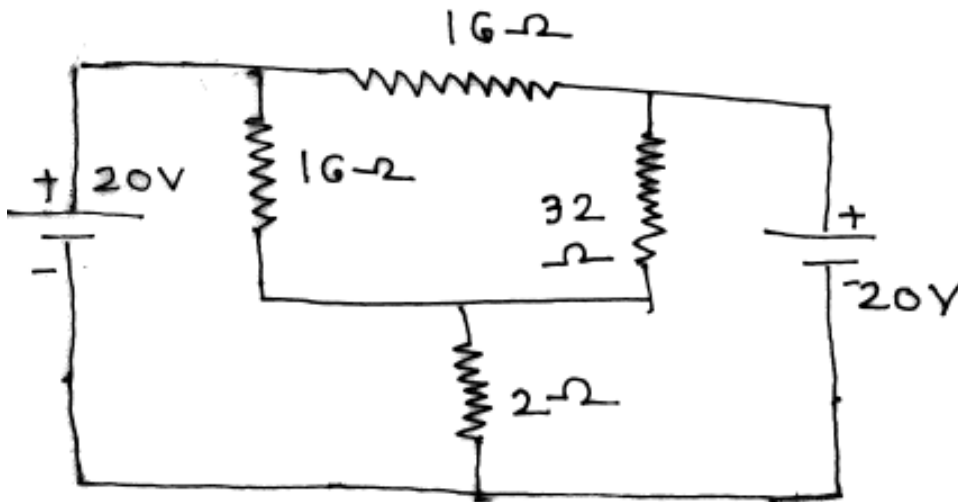


Fig. 1 Q. 3 (b)

OR

4. a) Calculate current flowing in  $2\Omega$  resistance and  $32\Omega$  resistance applying Kirchhoff's laws for the circuit shown in Fig. 1.

8

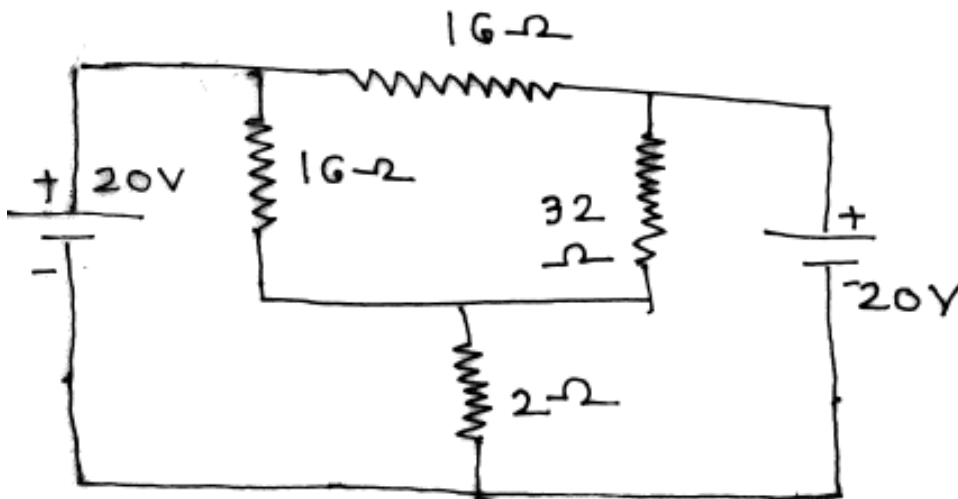


Fig. 1 Q. 4 (a)

- b) Derive the formulae to convert Delta connected network into its equivalent star connected network.

8



5. a) Define following terms and state its unit.
- i) Magnetic flux
  - ii) Magnetic flux density
  - iii) Permeability
  - iv) Magnetic field strength and
  - v) Reluctance. 10
- b) A ring has diameter of 21 cm and cross sectional area of  $10 \text{ cm}^2$ . The ring is made up of semi-circular sections of cast iron and cast steel. Find the amp-turns required to produce flux of  $8 \times 10^{-4} \text{ wb}$ . The relative permeabilities of cast steel and cast iron are 800 and 166 respectively. 8

OR

6. a) Derive expression for the energy stored per unit volume in the magnetic field. 6
- b) Compare electric and magnetic circuit. 6
- c) Define :
- i) Self inductance
  - ii) Mutual inductance and
  - iii) Coefficient of coupling. 6

SECTION – II

7. a) Derive the expression for energy stored in a capacitor. 6
- b) Derive an expression for RMS value of the sinusoidally varying current in terms of peak value. 6
- c) Sketch the following wave forms
- i)  $v = 280 \sin (100 \pi t + 90^\circ)$  and
  - ii)  $i = 7.07 \sin (100 \pi t + 30^\circ)$ . 4

OR

8. a) At the instant  $t = 0$ , the instantaneous value of a 50 Hz sinusoidal current is 6 Amp and increases further. Its rms value is 12 Amp.
- i) Write the expression for its instantaneous value
  - ii) Find the current at  $t = 0.01 \text{ s}$  and  $t = 0.015 \text{ s}$  and
  - iii) Sketch the wave form. 8
- b) Define as related to electrostatic
- i) Electric flux density
  - ii) Permittivity
  - iii) Dielectric strength and
  - iv) Capacitance. 8



9. a) When a 100 V is applied to a Coil A the current taken is 8 A and the power consumed is 120 Watt. When 100 V is applied to Coil B, the current drawn is 10 A and the power consumed is 500 Watt. Calculate the current and power when Coil A and Coil B are connected in series across 100 V supply. **10**

b) An impedance of  $(7 + j5) \Omega$  is connected in parallel with another impedance of  $(10 - j8) \Omega$  across a 230 V, 50 Hz supply. Calculate i) admittance, conductance and susceptance of the combined circuit ii) total current and p.f. **8**

OR

10. a) A series circuit consisting of  $25 \Omega$  resistor, 64 mH inductor and  $80 \mu\text{F}$  capacitor is connected to a 110 V, 50 Hz single phase supply. Calculate the current, voltage across each element and over all p.f. of the circuit and draw the phasor diagram. **10**

b) A parallel circuit consist of two branches. Branch i) consist of R of  $100 \Omega$  connected in series with inductance of 1 H and branch ii) consist of R of  $50 \Omega$  in series with capacitance of  $79.5 \mu\text{F}$ . This parallel circuit is connected across single phase 200 V, 50 Hz supply. Calculate  
i) Branch currents and total current drawn by circuit and  
ii) Total power consumed by circuit. **8**

11. a) Write short note on :  
i) Losses taking place in transformer and  
ii) Auto transformer. **12**

b) Define :  
i) Phase sequence and  
ii) Balanced load as referred to polyphase circuits. **4**

OR

12. a) Three coils each with resist. of  $12 \Omega$  an inductive reactance of  $5 \Omega$  are connected in star across 3 phase 400 V 50 Hz supply. Calculate power consumed. If same coils are then connected in delta then calculate the total power consumed. **12**

b) Differentiate core type and shell type transformer. **4**