

Total No. of Questions—12]

[Total No. of Printed Pages—4

Seat No.	
-------------	--

[4856]-14

F.E. (First Semester) EXAMINATION, 2015

BASIC ELECTRICAL ENGINEERING

(2008 PATTERN)

Time : Three Hours

Maximum Marks : 100

N.B. :- (i) Answer Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4, Q. No. 5 or Q. No. 6 from Section I; Q. No. 7 or Q. No. 8 Q. No. 9 or Q. No. 10, Q. No. 11 or Q. No. 12 from Section II.

(ii) Answers to the two Sections must be written in separate answer-books

(iii) Figures to the right indicate full marks.

(iv) Neat diagrams must be drawn wherever necessary.

(v) Use of non-programmable pocket size scientific calculator is permitted.

(vi) Assume suitable additional data, if necessary.

SECTION I

1. (a) What is insulation resistance ? State its unit and derive expression for insulation resistance of the single core cable. [8]
- (b) With neat diagram explain construction and working of lead acid cell. [8]

P.T.O.

Or

2. (a) A resistance element having cross sectional area of 10 mm^2 and length of 10 m takes a current of 4 amp from 200 V supply at temperature of 25°C . Find :
Resistivity of material and current it will take when temp. rises to 75°C . Assume $\alpha_{25} = 0.0003/^\circ\text{C}$. [10]
- (b) State applications of Ni-Iron cell and Nickel-Cadmium cell. [6]

3. (a) State and explain Kirchoff's Laws. [8]
- (b) Derive formula to convert delta connected network into star connected network. [10]

Or

4. (a) State and explain maximum power transfer theorem with example. [8]
- (b) State and explain superposition theorem with example. [10]
5. (a) Compare electric and magnetic circuits. [8]
- (b) Derive the equation $L = N^2/S$. Where L = self-induced e.m.f. of coil; N = no. of turns of coil; S = reluctance of magnetic circuit. [8]

Or

6. (a) Explain what do you mean by statistically induced e.m.f. and dynamically induced e.m.f. [6]
- (b) A steel ring of 25 cm mean diameter and circular cross section 3 cm diameter has an airgap of 1.5 mm length is wound uniformly with 700 turns of wire carrying a current of 2 amp. Calculate :
(a) MMF

- (b) Flux density
- (c) Reluctance
- (d) Relative permeability of steel ring. [10]

SECTION II

7. (a) Define with respect to alternating quantities : [4]
- (i) Form factor
 - (ii) Crest factor
- (b) Sketch waveform of current and find its r.m.s. value and average value for the equation : [12]
- (i) $i_1 = 15 \sin (314.159t)$
 - (ii) $i_2 = 10 \sin (314.159t) - \pi/2$

Or

8. (a) Derive an expression for average value of alternating current. [8]
- (b) Derive an expression for energy stored in a capacitor. [8]

9. (a) Define :
- (i) Admittance
 - (ii) Conductance
 - (iii) Susceptance

Express admittance in rectangular and polar form. State unit of admittance and draw admittance triangle. [9]

- (b) A circuit consisting of resistance of 20Ω and inductance of 0.1 H is connected in series across single phase, 200 V , 50 Hz supply. Calculate : [9]
- (i) Impedance

- (ii) Current drawn
- (iii) Power consumed
- (iv) Draw phasor diagram.

Or

- 10.** (a) If a sinusoidal voltage $v = V_m \sin \omega t$ is applied across R-L series circuit. Derive expression for current and average power consumed by a circuit. Draw waveform of power. [9]
- (b) Two impedances $Z_1 = 12 + j16 \Omega$ and $Z_2 = 8 - j4 \Omega$ are connected in parallel across the voltage of 23 V. Calculate :
- (i) Total current drawn
 - (ii) Total power
 - (iii) Overall power factor of the circuit [9]
- 11.** (a) Derive an expression for e.m.f. induced in the transformer. [8]
- (b) 25 kVA, 50 Hz single phase transformer has an iron loss and full load copper loss of 350 W and 400 W respectively. Find efficiency at 50% of full load at unity power factor. [8]

Or

- 12.** (a) Explain advantages of 3 phase system over single phase system. [6]
- (b) A balanced star connected load is supplied by 3-phase, 415 V, 50 Hz supply. Current in phase is 20 A and lags 30° behind phase voltage. Find : [10]
- (i) Power consumed by load
 - (ii) Circuit parameters
 - (iii) Load power factor.