

Total No. of Questions : 6]

SEAT No. :

**P657**

[4456]-12

[Total No. of Pages : 2

**F.E. (Semester - II)**

**BASIC ELECTRONICS ENGINEERING**

**(2008 Course)**

*Time : 2 Hours]*

*[Max. Marks : 50*

*Instructions to the candidates:*

- 1) Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Use of logarithmic tables slide rule, Mollier charts, electronic pocket calculator and steam tables is allowed.
- 5) Assume suitable data, if necessary.

**Q1)** a) Explain how DC output voltage of a full wave rectifier is improved when capacitor filter is used? Draw the waveforms of load voltage and diode current. **[8]**

b) Define  $\alpha_{dc}$  and  $\beta_{dc}$  of a transistor. For a transistor the base current is 100  $\mu$ A and collector current is 2.9mA. Find  $\alpha_{dc}$  and  $\beta_{dc}$  **[8]**

OR

**Q2)** a) A diode whose internal resistance is 20 ohms is to supply to 1000 ohms load from a 110V rms source of supply, Calculate: **[6]**

- i) Peak load current
- ii) DC load current
- iii) AC load current
- iv) DC load voltage

b) Explain BJT as a switch and draw the necessary waveforms. **[4]**

c) Compare SCR and TRIAC. **[6]**

**Q3)** a) An op-amp is used in non-inverting mode with  $R_1 = 1K\Omega$ ,  $R_F = 12K\Omega$ ,  $V_{cc} = \pm 15V$ . Calculate output voltage for **[6]**

- i)  $V_{in} = 250mV$
- ii)  $V_{in} = 3V$

**P.T.O.**

- b) Implement the following Boolean expression using both NAND and NOR gates. [6]
- i)  $\overline{A}BC + AC + B\overline{C}D$
- ii)  $AB + C\overline{D} + AD + BC$
- c) State difference between Synchronous and Asynchronous Counters.[4]

OR

- Q4)** a) Draw block diagram of Op-Amp and explain. [6]
- b) For inverting summing amplifier, if following inputs are applied, then calculate output voltage.  
 $V_1 = 1.5V, V_2 = 3.5V$  and  $R_1 = R_2 = R_f = 5.2 \text{ K}\Omega$  [4]
- c) What is multiplexer? What is the relation between number of select lines and inputs? Draw diagram of 4:1 Mux and explain significance of strobe pin. [6]

- Q5)** a) Draw block diagram of Electronic weighing machine and explain its operation. [6]
- b) What is RTD? Draw its constructional diagram and explain its operation. [6]
- c) What is the need of modulation? Explain Amplitude modulation in detail. [6]

OR

- Q6)** a) Write short note on any two : [6]
- i) PLC system
- ii) Active - passive Transducer
- iii) Thermocouple
- iv) Piezoelectric Transducer
- b) Draw and explain block diagram of Mobile Communication system. Explain concept of cellular. [6]
- c) Write short note on Co-axial cable and fiber optic cable. [6]

