

Total No. of Questions—6]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

[4856]-26

F.E. (Second Semester) EXAMINATION, 2015

BASIC ELECTRONICS ENGINEERING

(2008 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Solve Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4, Q. No. 5 or Q. No. 6.

(ii) Figures to the right indicate full marks.

(iii) Neat diagrams must be drawn wherever necessary.

(iv) Assume suitable data, if necessary.

1. (a) Draw a neat circuit diagram of Bridge Rectifier with capacitor filter and explain its operation with waveforms. Give the equation of output voltage with and without capacitor filter. [7]

(b) Discuss the effect of the following capacitors on frequency response of amplifier. [6]

(1) Coupling capacitor

(2) Bypass capacitor

(3) Diffusion capacitor.

(c) Give and explain any *four* features of SCR. [4]

P.T.O.

Or

2. (a) Draw and explain circuit diagram of single stage CE amplifier. Draw a frequency response and explain it with gain, lower and higher frequencies. [7]
- (b) Compare half wave and full wave rectifier. [6]
- (c) For the circuit shown in the figure below, find : [4]
- (1) O/P voltage
- (2) Voltage across R_s .

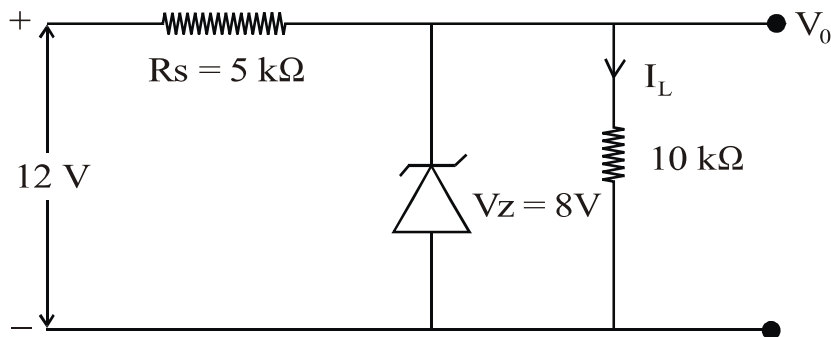


Fig.

3. (a) Explain the following ideal characteristics of OP-Amp. [6]
- (1) CMRR
- (2) Slew Rate
- (3) Band-width
- (b) Draw the diagram of 8 : 1 Mux. What is the relation between number of select lines and Input ? Give applications of multiplexers. [7]
- (c) State and prove De Morgan's theorem. [4]

Or

4. (a) Draw and explain circuit diagram of square wave Generator using Op-Amp. [7]

(b) Simplify the following expression. [6]

$$Y = \overline{(\overline{AB} + \overline{A} + AB)}$$

(c) Explain any *four* characteristics of an Ideal Op-Amp. [4]

5. (a) Explain different characteristics of Transducer. [6]

(b) Draw and explain Superheterodyne Receiver. [6]

(c) Write a short note on any *one* : [4]

(1) Electronic Weighing Machine.

(2) PLC.

Or

6. (a) With neat diagram explain construction and working of LVDT. [6]

(b) Draw and explain block diagram of mobile communication system. [6]

(c) Write a short note on any *one* : [4]

(1) Fiber Optic Cable

(2) Co-axial cable.