

UNIVERSITY OF PUNE
[4361]-105
F. E. Examination – 2013
BASIC ELECTRONICS ENGINEERING
(2012 Pattern)

[Time : 2 Hours]

[Max. Marks : 50]


Total No. of Questions : 08

[Total No. of Printed Pages :3]

Instructions :

- (1) Black figures to the right indicate full marks.
- (2) Use of logarithmic tables, slide rule, Mollier charts, electronic pocket calculator and steam tables is allowed.
- (3) Assume suitable data, if necessary.

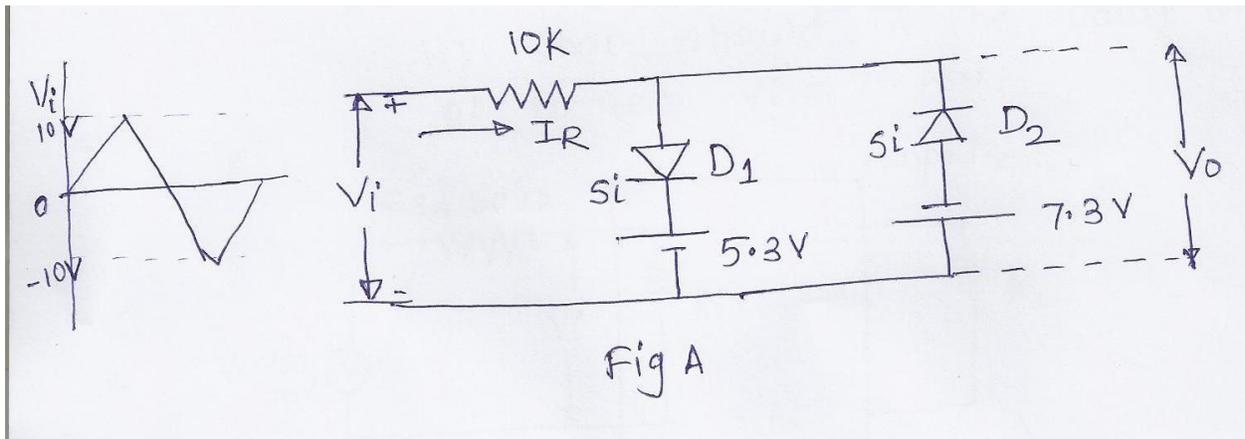Q1) A) Sketch I_R and V_o w. r. t time for the network shown in fig. A. [06]
Assume both the diodes are silicon type with $V_f = 0.7$ V



B) For a BJT as a switch why CB and cc configurations are not preferred. [02]

C) Explain how R_i and R_o affect the performance of the BJT voltage amplifier. [04]


OR

Q2) A) Explain with V-I characteristics the working of zener diode as voltage regulator. [06]

B) In the voltage amplifier shown in Fig B, $V_s=100\text{mV}$ $R_s=50\ \Omega$ [06]

i) Calculate input voltage V_i if the input resistance R_i is $600\ \Omega$

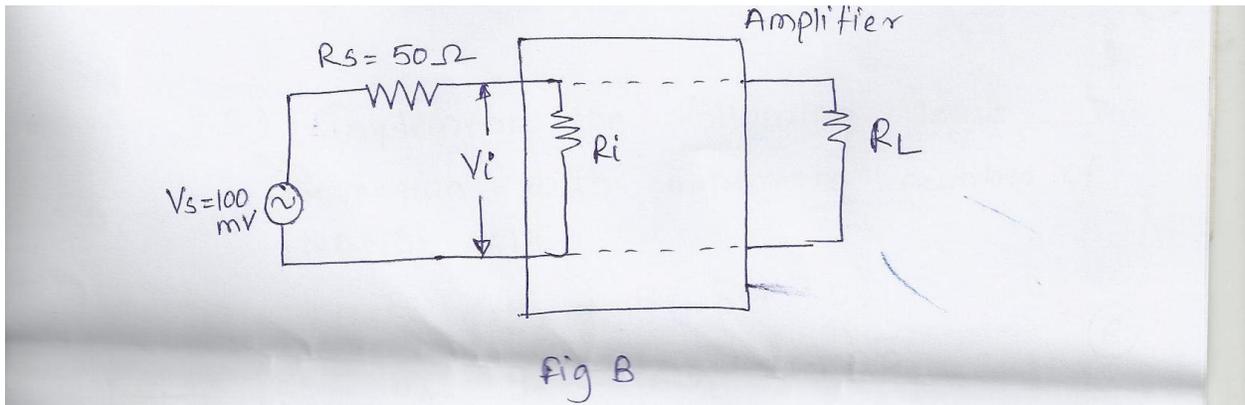
ii) What should be the value of R_i to get $V_i = 75\ \text{mV}$



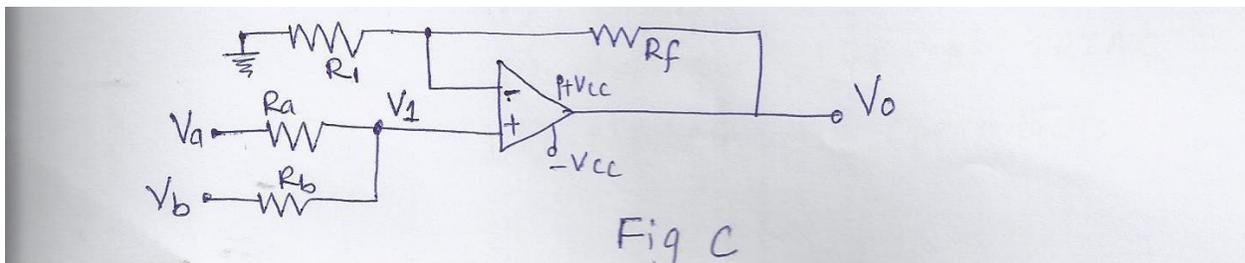Q3) A) In fig. C if $V_a = +2\text{V}$ $V_b = +4\text{V}$ [04]

$R_a = R_b = R_1 = 1\ \text{k}\ \Omega$ and $R_f = 3\ \text{k}\ \Omega$

determine the voltage V_1 at non-inverting terminal of OP-AMP and output voltage V_o



B) Draw the block diagram of full adder using two half adder, explain its working with proper expression for sum and carry [06]

C) Explain how EX-OR gate can be used as an inverter. [02]

OR

Q4) A) With neat waveform explain IC555 in astable mode. [06]

B) Implement the following logic expression with minimum number of NAND gate. [06]

i) $y_1 = B (\overline{D} + \overline{C}D)$

ii) $y_2 = AB + CD + B\overline{C}$

Q5) A) Explain in detail, the selection criteria for transducer. [06]

B) Explain in detail [07]

i) construction of TRIAC

ii) characteristics of TRIAC

iii) modes of operation

OR

Q6) A) Explain with block diagram an electronic weighing machine. [06]

B) Explain the construction of DIAC w.r.t [07]

i) Characteristics

ii) Application

Q7) A) What is the importance of modulation index. Draw the AM waveform for [08]

i) Linear modulation

ii) Over modulation

iii) Modulation index = 0

B) Explain the basic structure of mobile phone system. [05]

OR

Q8) A) With respect to FM explain [08]

i) Frequency deviation

ii) Modulation index

iii) Deviation ratio

iv) Frequency spectrum of FM

B) Write a note on co-axial cable and optical fibre cable. [05]